


4A237021 晶片二甲 葉聖翔

1. 大多數家庭所使用的實心銅電線直徑為 1.63mm ，求出此種直徑的實心銅電線 50m 的電阻值。(銅的電阻率為 $1.723 \times 10^{-8} \Omega \cdot \text{m}$)

(A) 0.412Ω

$$R = \rho \times \frac{L}{A} = 1.723 \times 10^{-8} \times \frac{50}{\pi \left(\frac{1.63 \times 10^{-3}}{2} \right)^2} = 0.4128 \Omega$$

2. 如圖中所示電路節點 V_1 及 V_2 的電壓值，各為多少伏特？

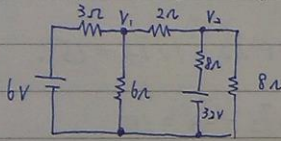

$$V_1 \text{ 的 KCL: } \frac{V_1 - 6}{3} + \frac{V_1}{6} + \frac{V_1 - V_2}{2} = 0$$


$$\Rightarrow \left(\frac{1}{3} + \frac{1}{6} + \frac{1}{2} \right) V_1 - \frac{1}{2} V_2 - \frac{6}{3} = 0 \quad \text{--- (1)}$$

$$V_2 \text{ 的 KCL: } \frac{V_2 - V_1}{2} + \frac{V_2 - 32}{8} + \frac{V_2}{8} = 0$$

$$\Rightarrow \left(\frac{1}{2} + \frac{1}{8} + \frac{1}{8} \right) V_2 - \frac{1}{2} V_1 - \frac{32}{8} = 0 \quad \text{--- (2)}$$


將 (1)(2) 聯立解得， $V_1 = 7\text{V}$ ， $V_2 = 10\text{V}$

3. 如圖所示，當開關 S 閉合，電流 I 為多少？

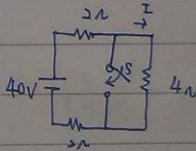

當開關閉合時， 4Ω 因被短路而兩端等電路，故無電流 0A 。

4. 圖中 I 為？

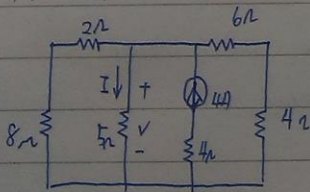


$$I = \frac{\frac{40}{5}}{\frac{1}{2+8} + \frac{1}{5} + \frac{1}{6+4}} \times 4 = 2\text{A}$$

5. 圖中之電路，以迴路分析法所列出之方程式如下：

$$\begin{aligned} a_{11}I_1 + a_{12}I_2 + a_{13}I_3 &= 15 \\ a_{21}I_1 + a_{22}I_2 + a_{23}I_3 &= 10 \\ a_{31}I_1 + a_{32}I_2 + a_{33}I_3 &= -10 \end{aligned}$$

則 $a_{11} + a_{22} + a_{33} = ?$

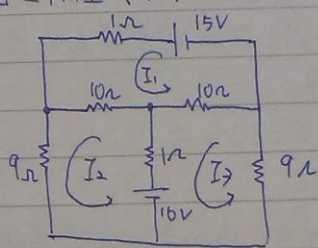

第一迴路的KVL方程式 = $(1+10+10)I_1 - 10I_2 - 10I_3 = 15$,


第二迴路的KVL方程式 = $-10I_1 + (1+10+9)I_2 - I_3 = 10$

第三迴路的KVL方程式 = $-10I_1 - I_2 + (9+10+1)I_3 = -10$

$a_{11} = 21, a_{22} = 20, a_{33} = 20$


因此， $a_{11} + a_{22} + a_{33} = 61$

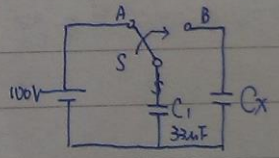6. 如圖所示， C_1 為 $33\mu F$ 充滿電後，把開關 S 由 A 移至 B ，則 C_1 之電壓降為 $75V$ 後達到穩定。假設 C_x 之初始電壓值為 0 ，則 C_x 為？



$$75 = \frac{100C_1}{C_1 + C_x} \Rightarrow 75C_x = 25C_1 \Rightarrow C_x = \frac{1}{3}C_1 = 11\mu F$$

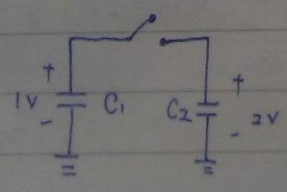7. In the figure, $C_1 = 2\mu F, C_2 = 1\mu F$, derive the voltage on C_1 and C_2 after the switch T_s is turned on?



$$\begin{aligned} Q_T &= C_1V_1 + C_2V_2 = (C_1 + C_2)V \\ \Rightarrow V &= \frac{C_1V_1 + C_2V_2}{C_1 + C_2} = \frac{2 \times 1 + 1 \times 2}{2 + 1} = \frac{4}{3} V \end{aligned}$$

8. 如圖所示，開關打開一段很長時間，在 $t=0$ 時開關瞬間閉合，則 $t \geq 0$ 時，求 $V_c(t) = ?$


時間常數 $RC = [(15 \parallel 10) + 4] \times 10^3 \times 10^{-6} = 10^{-2} \text{ Sec}$ ，初值 $V_c = 0$

終值：電容器已開路，利用分壓律 $V_c(t \rightarrow \infty)$

$$= 40 \times \frac{10}{15+10} = 16 \text{ V}$$

$$\Rightarrow V_c(t) = (0-16)e^{-t/RC} + 16 = 16(1 - e^{-100t}) \text{ V}$$

9. 如圖所示之 RC 並聯電路，其相量 I 為？

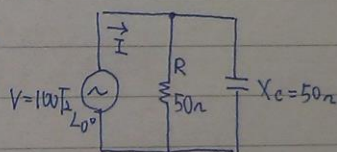

$$Z = R \parallel (-jX_c) = \frac{R(-jX_c)}{R - jX_c} = \frac{-j2500}{50 - j50} = \frac{2500 \angle -90^\circ}{50\sqrt{2} \angle -45^\circ} = \frac{50 \angle -45^\circ}{\sqrt{2}}$$

$$\Rightarrow I = \frac{V}{Z} = \frac{100\sqrt{2} \angle 0^\circ}{\frac{50 \angle -45^\circ}{\sqrt{2}}} = \frac{100\sqrt{2} \angle 0^\circ}{50\sqrt{2} \angle -45^\circ} = 4 \angle 45^\circ \text{ A}$$

或

$$I = \frac{100\sqrt{2} \angle 0^\circ}{50} + \frac{100\sqrt{2} \angle 0^\circ}{-j50} = 2\sqrt{2} \angle 0^\circ + 2\sqrt{2} \angle 90^\circ = 4 \angle 45^\circ \text{ A}$$

10. 图中 $C = 1\mu F$, 当 $t=0$ 时将开关接上。若电容初值 $= 5V$, 求

(a) 电容的电流与时间关系式

(b) $t = 3 \times 10^{-5}$ 秒的端电压

Sol:


(a) 时间常数 $RC = 30 \times 10^{-6} \text{ Sec} = 3 \times 10^{-5} \text{ Sec}$. 则

$$V_c(t) = V_{c0} \times e^{-t/RC} = 5 \times 10^{-5} t / 3 \text{ V}$$


$$\begin{aligned} \Rightarrow i(t) &= -i_c(t) = -C \frac{dV_c(t)}{dt} = \frac{10^5}{3} \times 10^{-6} \times 5 e^{-10^5 t / 3} \\ &= \frac{1}{6} e^{-10^5 t / 3} \end{aligned}$$

(b) $V_c(t=3 \times 10^{-5}) = 5 \times e^{-10^5 \times (3 \times 10^{-5}) / 3} = 5 \times 10^{-1} \text{ V}$

11. 如图所示, $I = ?$

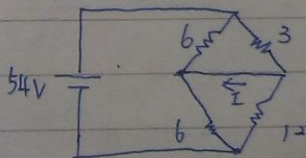

$$R = (6/3) + (6/12) = 2 + 4 = 6\Omega$$

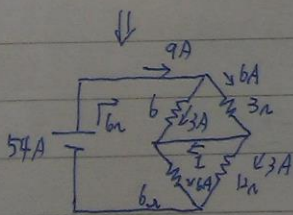

$$I = 6 - 3 = 3A$$

12. What is the difference between drift current and diffusion current?

Sol:

漂移电流是因为电位不均而有电场存在所产生的

扩散电流则是因为载子浓度不均所产生的