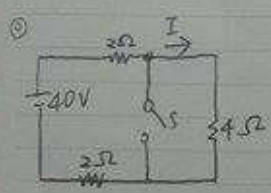



$$\begin{cases} \frac{V_1 - 6}{3} + \frac{V_1}{6} + \frac{V_1 - V_2}{2} = 0 \\ \frac{V_2 - V_1}{2} + \frac{V_2 - 3}{8} + \frac{V_2}{8} = 0 \end{cases}$$

$$\begin{cases} 2V_1 - 12 + V_1 + 3V_1 - 3V_2 = 0 \\ 4V_2 - 4V_1 + V_2 - 3 + V_2 = 0 \end{cases}$$

$$\begin{cases} 6V_1 - 3V_2 = 12 \\ -4V_1 + 6V_2 = 3 \end{cases} \quad \begin{cases} 2V_1 - V_2 = 4 \\ -2V_1 + 3V_2 = 16 \end{cases} \quad \begin{cases} 2V_2 = 20, V_2 = 10 \\ V_1 = 7V_2 \end{cases}$$




當S合開後  
4Ω 短路  
I=0.

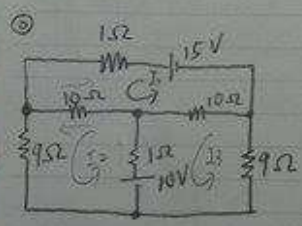

$$\begin{cases} a_{11}I_1 + a_{12}I_2 + a_{13}I_3 = 15 \\ a_{21}I_1 + a_{22}I_2 + a_{23}I_3 = -10 \\ a_{31}I_1 + a_{32}I_2 + a_{33}I_3 = -10 \end{cases} \quad a_{11} + a_{22} + a_{33} = ?$$

$$\begin{cases} -15 + I_1 + 10I_1 + 10I_1 - 10I_2 - 10I_3 = 0 & 21I_1 - 10I_2 - 10I_3 = 15 \\ 20I_2 - 10I_3 - 10I_1 = 0 & -10I_1 + 20I_2 - I_3 = +10 \\ 20I_3 + 10I_2 - 10I_1 = 0 & -10I_1 - I_2 + 20I_3 = 10 \end{cases}$$
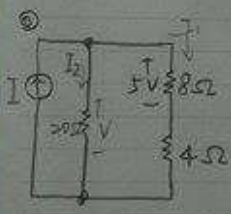
$$a_{11} + a_{22} + a_{33} = 21 + 20 + 20 = 61 \neq$$





$$I_1 = \frac{V}{R} = \frac{5}{8}$$

$$I_2 = \frac{7.5}{20} = \frac{1.5}{4}$$


$$I = \frac{5}{8} + \frac{1.5}{4} = \frac{5}{8} + \frac{3}{8} = \frac{8}{8} = 1A$$
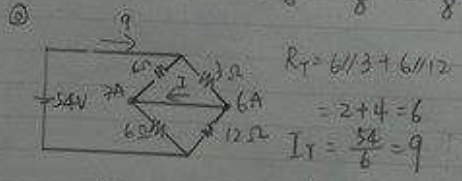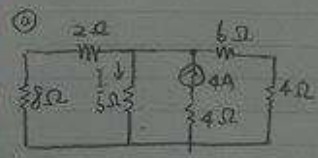
$$V_T = \frac{5}{2} + 5 = 2.5 + 5 = 7.5$$




$$R_T = 6 // 3 + 6 // 12 = 2 + 4 = 6$$

$$I_T = \frac{5A}{6} = 9$$

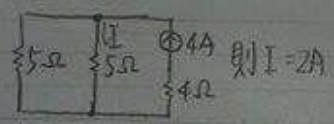


則 I = 2A

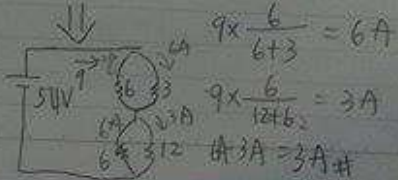


$$9 \times \frac{6}{6+3} = 6A$$

$$9 \times \frac{6}{12+6} = 3A$$


$$6A - 3A = 3A \neq$$

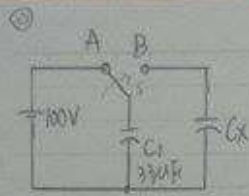

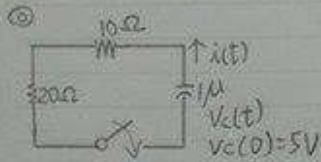
①  $C_1$  75V 連接態,  $S \rightarrow B$   
 $Q = CV$   
 $(C_x + C_1) 75V = 100V \times C_1$   
 $75C_x = 25C_1, C_x = 11\mu F$



② (a)  $\tau = RC = 30 \times 10^{-6} = 3 \times 10^{-5}$   
 $V_c(t) = V_{c0} \cdot e^{-\frac{t}{\tau}}$   
 $= 5 \times e^{-\frac{t}{3 \times 10^{-5}}}$   
 $i(t) = -C \frac{dV_c(t)}{dt} = \frac{10^5}{3} \times 10^{-6} \times 5 e^{-10^5 t / 3} = \frac{1}{6} e^{-10^5 t / 3}$   
 (b)  $\tau = 3 \times 10^{-5}$   
 $V_{c0} (3 \times 10^{-5}) = 5 \times e^{-\frac{3 \times 10^{-5}}{3 \times 10^{-5}}}$   
 $= 5 \times e^{-1} = \frac{5}{e}$

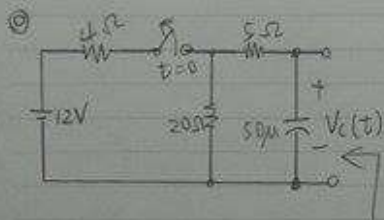

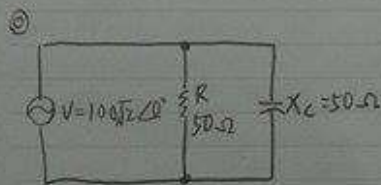③  $R_T = 20 + 5 = 25$   
 $\tau = RC = 25 \times 50 \times 10^{-6} = 1.25 \times 10^{-3}$   
 $V = \frac{20}{20+5} \times 12 = 10V$   
 $V_c(t) = (10 - 0) \times e^{-\frac{t}{\tau}}$   
 $= 10 \times e^{-\frac{t}{1.25 \times 10^{-3}}} = 10 e^{-800t}$



④  $Z = \frac{R \cdot jC}{R + jC} = \frac{50 \times 50 \angle -90}{50 - j50} = \frac{2500 \angle -90}{50\sqrt{2} \angle -45} = \frac{50 \angle -45}{\sqrt{2}}$   
 $I = \frac{V}{Z} = \frac{100\sqrt{2} \angle 0}{\frac{50 \angle -45}{\sqrt{2}}} = \frac{200 \angle 0}{50 \angle -45} = 4 \angle 45$

⑤ 純矽晶體, 在室溫下載子濃度為  $P = n = 1.45 \times 10^{10}$  個/cm<sup>3</sup>,  $\mu_n = 1500$  cm<sup>2</sup>/V·s,  $\mu_p = 480$  cm<sup>2</sup>/V·s, 求導電率及 R

$$\sigma = 1.6 \times 10^{-19} \times 1.45 \times 10^{10} \times (1500 + 480) = 4.59 \times 10^{-6} \text{ S/cm}$$

$$\rho = \frac{1}{\sigma} = \frac{1}{4.59 \times 10^{-6}} \approx 2.2 \times 10^5 \Omega \cdot \text{cm}$$

⑥  $n_i = 1.5 \times 10^{10}$  /cm<sup>3</sup>, 原子密度為  $5 \times 10^{23}$  /cm<sup>3</sup>, 若  $10^9$  個的原子摻入 1 個施體 (P) 則電洞?

$$N_D = \frac{5 \times 10^{23}}{10^9} = 5 \times 10^{14}$$

$$\rho = \frac{n_i^2}{N_D} = \frac{(1.5 \times 10^{10})^2}{5 \times 10^{14}} = 4.5 \times 10^6$$